





دانشگاه صنعتی امیرکبیر
دانشکده مهندسی برق

طراحی مدارهای VLSI

فصل چهارم: واورنگر CMOS

مجید شالچیان

majid.shalchian@gmail.com

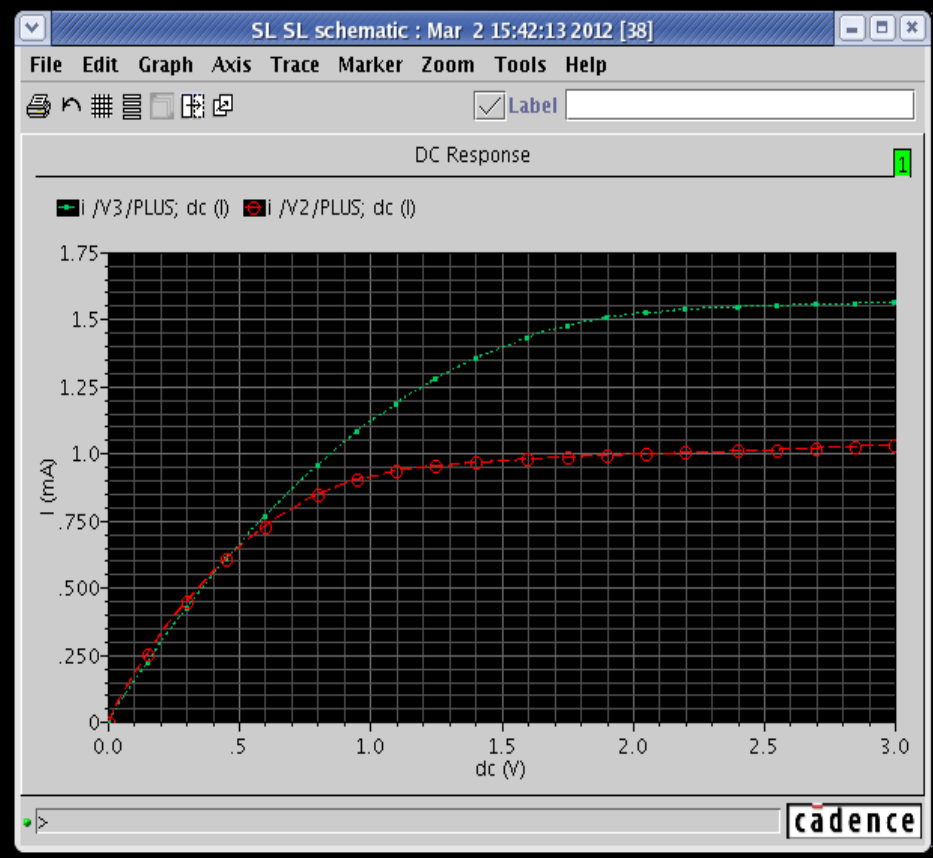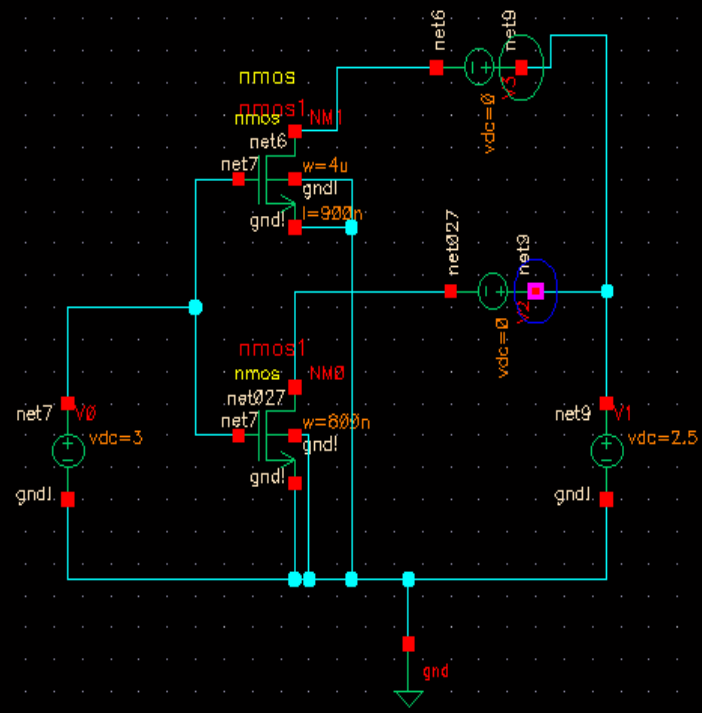

mouse L: mouseSingleSelectPt M: mousePopUp() R:sevDirectPlot('sevSession1 'asiDirectPlotResultsMenuC


Select Instance Terminal... (Hit Escape to quit)

ترانزیستور انتقالی

• در ترانزیستور انتقالی مقدار ولتاژ خروجی چقدر است؟

• فرض کنیم خروجی برابر V_{DD} باشد. در این حالت چون



 
$V_{GS}=0 < V_t$ است ترانزیستور قطع می شود.




پس برای آنکه ترانزیستور روشن بماند حداکثر ولتاژ خروجی آن

برابر $V_{DD} - V_t$ خواهد شد.

   
به همین دلیل می گوییم ترانزیستور nMOS مقدار منطقی ۱ را خوب عبور نمی دهد.



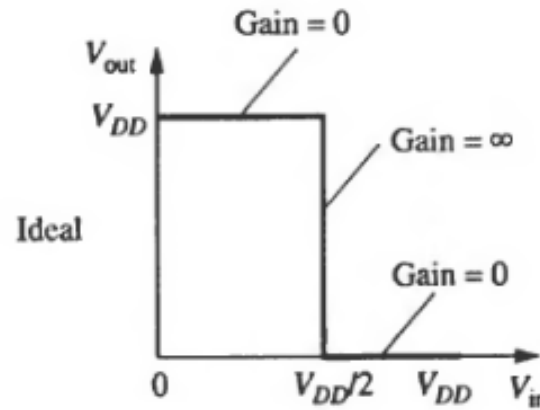- مقدمه
- مشخصه انتقالی
- رفتار ایستا
- رفتار پویا
- تحلیل توان، انرژی و طراحی برای مصرف کم







(a)

 

(b)

مشخصه واقعی تر و وارونگر

   

 



$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$



پیاده سازی با منطق CMOS ایستا

• در منطق CMOS ایستا خروجی همواره یک مسیر مقاومتی به V_{DD} یا زمین دارد.

  • وارونگر پایه مدارهای منطقی ترکیبی CMOS ایستا است.



آنالیز مرتبه اول حالت ایستا

  

$$V_{OL} = 0$$
$$V_{OH} = V_{DD}$$


- ❑ Full rail-to-rail swing \Rightarrow high noise margins
 - Logic levels not dependent upon the relative device sizes \Rightarrow transistors can be minimum size \Rightarrow ratioless
- ❑ Always a path to V_{dd} or GND in steady state \Rightarrow low output impedance (output resistance in $k\Omega$ range) \Rightarrow large fan-out (albeit with degraded performance)
- ❑ Extremely high input resistance (gate of MOS transistor is near perfect insulator) \Rightarrow nearly zero steady-state input current
- ❑ No direct path steady-state between power and ground \Rightarrow no static power dissipation
- ❑ Propagation delay function of load capacitance and resistance of transistors

- مقدمه
- مشخصه انتقالی
- رفتار ایستا
- رفتار پویا
- تحلیل توان، انرژی و طراحی برای مصرف کم

□ DC Response: V_{out} vs. V_{in} for a gate


□ Ex: Inverter

- When $V_{in} = 0$ $\rightarrow V_{out} = V_{DD}$
- When $V_{in} = V_{DD}$ $\rightarrow V_{out} = 0$
- In between, V_{out} depends on transistor size and current
- By KCL, must settle such that $I_{dsn} = |I_{dsp}|$
- We could solve equations
- But graphical solution gives more insight

 

- ❑ Current depends on region of transistor behavior
- ❑ For what V_{in} and V_{out} are nMOS and pMOS in
 - Cutoff?
 - Linear?
 - Saturation?

Cutoff	Linear	Saturated
$V_{gsn} <$	$V_{gsn} >$	$V_{gsn} >$
	$V_{dsn} <$	$V_{dsn} >$

 


Cutoff	Linear	Saturated
$V_{gsp} > V_{tp}$ $V_{in} > V_{DD} + V_{tp}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{DD} + V_{tp}$ $V_{dsp} > V_{gsp} - V_{tp}$ $V_{out} > V_{in} - V_{tp}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{DD} + V_{tp}$ $V_{dsp} < V_{gsp} - V_{tp}$ $V_{out} < V_{in} - V_{tp}$


$$V_{gsp} = V_{in} - V_{DD}$$

$$V_{tp} < 0$$

$$V_{dsp} = V_{out} - V_{DD}$$

 


Review: Short Channel I-V Plot (NMOS)

 

NMOS transistor, $0.25\mu\text{m}$, $L_d = 0.25\mu\text{m}$, $W/L = 1.5$, $V_{DD} = 2.5V$, $V_T = 0.4V$


Review: Short Channel I-V Plot (PMOS)

 - All polarities of all voltages and currents are reversed



PMOS transistor, $0.25\mu m$, $L_d = 0.25\mu m$, $W/L = 1.5$, $V_{DD} = 2.5V$, $V_T = -0.4V$

 - Make pMOS is wider than nMOS such that $\beta_n = \beta_p$





- Want common coordinate set V_{in} , V_{out} , and I_{Dn}


$$I_{DSp} = -I_{DSn}$$

$$V_{GSn} = V_{in} ; V_{GSp} = V_{in} - V_{DD}$$

 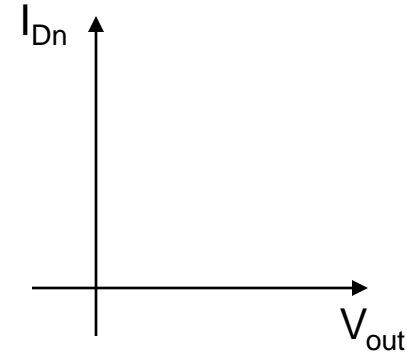
$$V_{DSn} = V_{out} ; V_{DSp} = V_{out} - V_{DD}$$



CMOS Inverter Load Lines

 


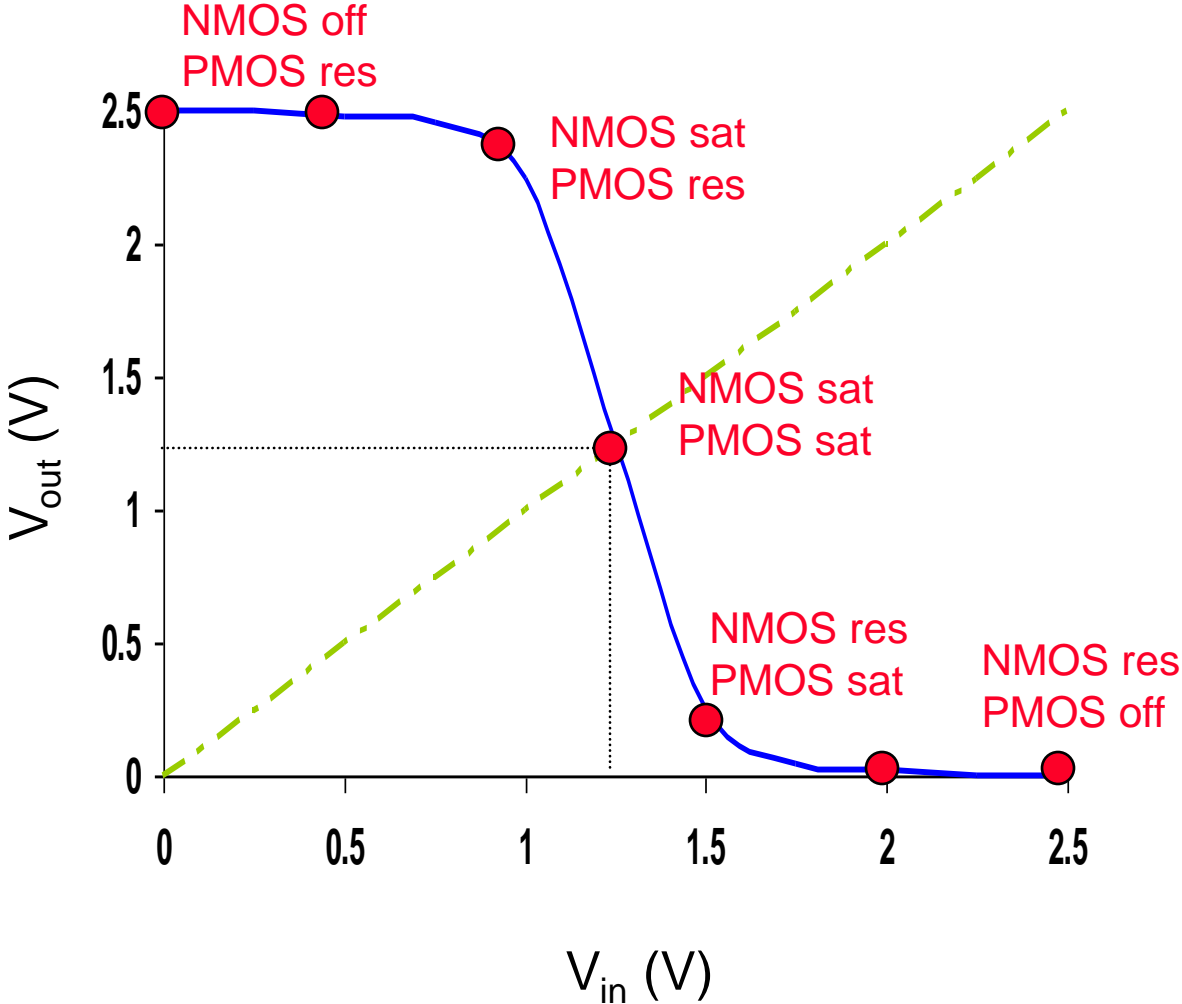0.25 μ m, $W/L_n = 1.5$, $W/L_p = 4.5$, $V_{DD} = 2.5V$, $V_{Tn} = 0.4V$, $V_{Tp} = -0.4V$




Operating Regions

- Revisit transistor operating regions

 

Region	nMOS	pMOS
A		
B		
C		
D		
E		

 


نواحی کار وارونگر با ساختار متقارن

$$k'_n = k'_p$$

$$V_{tn} = -V_{tp}$$

Region	Condition	p-device	n-device	Output
A	$0 \leq V_{in} < V_{tn}$	linear	cutoff	$V_{out} = V_{DD}$
B	$V_{tn} \leq V_{in} < V_{DD}/2$	linear	saturated	$V_{out} > V_{DD}/2$
C	$V_{in} = V_{DD}/2$	saturated	saturated	V_{out} drops sharply
D	$V_{DD}/2 < V_{in} \leq V_{DD} - V_{tp} $	saturated	linear	$V_{out} < V_{DD}/2$
E	$V_{in} > V_{DD} - V_{tp} $	cutoff	linear	$V_{out} = 0$

 

مقدمه

مشخصه انتقالی

رفتار ایستا


رفتار پویا

تحلیل توان، انرژی و طراحی برای مصرف کم

هدف از تحلیل ایستایی تحلیل پارامترهای استحکام وارونگر نظیر حاشیه نویز و بررسی اثر تغییر پارامترهای ابعادی روی مشخصه انتقالی ترانزیستور می باشد.

معمولا می خواهیم حاشیه نویز بیشینه و مشخصه انتقالی متقارن داشته باشیم

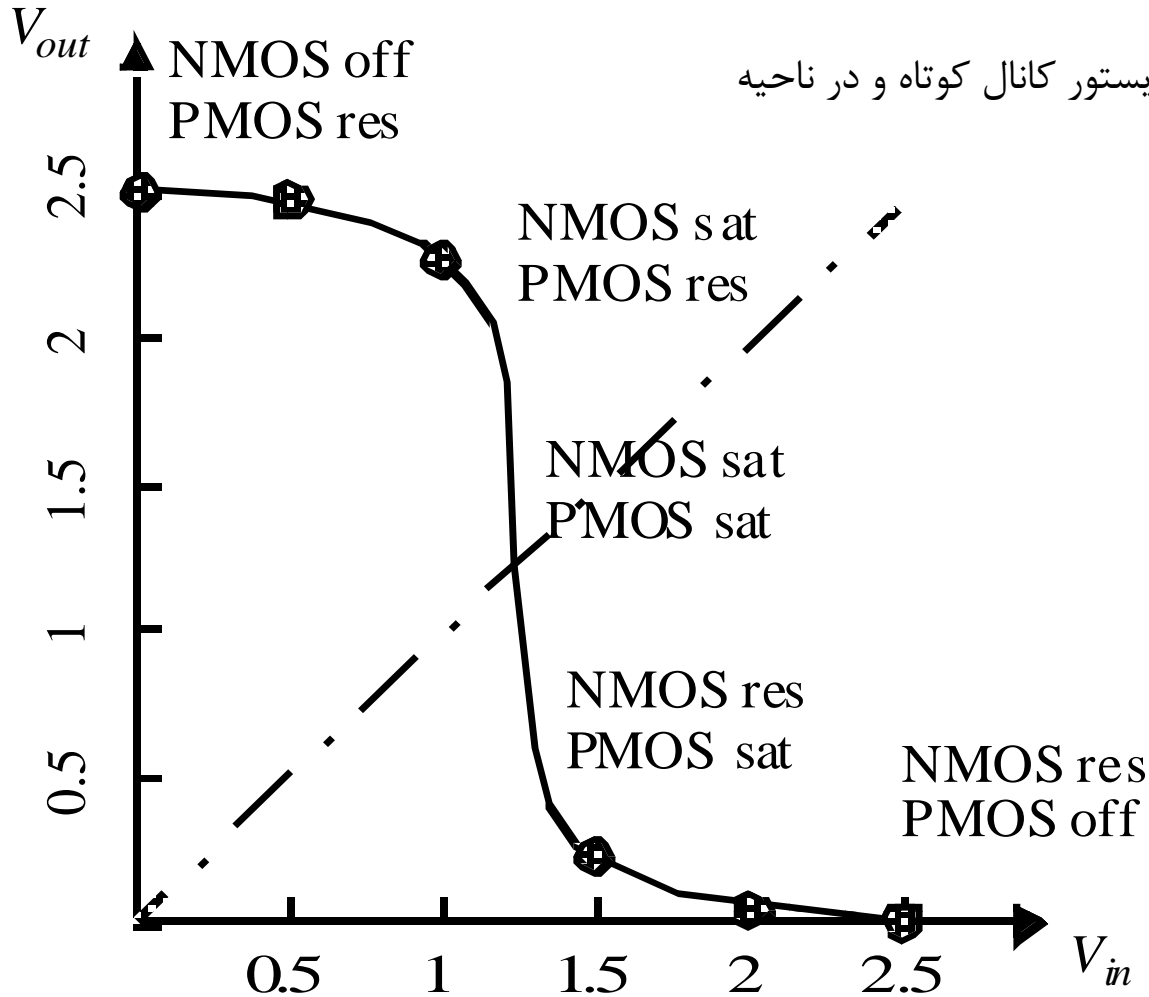۱- تحلیل نقطه آستانه سویچینگ VM ($V_{in}=V_{out}$)



$$k_n V_{DSATn} \left(V_M - V_{Tn} - \frac{V_{DSATn}}{2} \right) + k_p V_{DSATp} \left(V_M - V_{DD} - V_{Tp} - \frac{V_{DSATp}}{2} \right) = 0$$

Solving for V_M yields

$$V_M = \frac{\left(V_{Tn} + \frac{V_{DSATn}}{2} \right) + r \left(V_{DD} + V_{Tp} + \frac{V_{DSATp}}{2} \right)}{1 + r} \quad \text{with } r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}} = \frac{v_{satp} W_p}{v_{satn} W_n}$$

اگر فرض کنیم مقدار V_{DD} نسبت به ولتاژ آستانه و ولتاژ اشباع سرعت ترانزیستور ها بحد کافی بزرگ باشد.

R بیانگر قدرت درایو نسبی pmos نسبت به nmos است. اگر pMOS قویتر باشد

$$V_M \approx \frac{r V_{DD}}{1 + r}$$

VM از $V_{DD}/2$ زیادتر می شود و اگر NMOS قویتر باشد کمتر می شود.

$V_M = V_{DD}/2$ (to have comparable high and low noise margins), so want $r \approx 1$


$$\frac{(W/L)_p}{(W/L)_n} = \frac{k'_n V_{DSATn} (V_M - V_{Tn} - V_{DSATn}/2)}{k'_p V_{DSATp} (V_{DD} - V_M + V_{Tp} + V_{DSATp}/2)}$$

In our generic 0.25 micron CMOS process, using the process parameters from slide L03.25, a $V_{DD} = 2.5V$, and a minimum size NMOS device ($(W/L)_n$ of 1.5) □

	$V_{T0}(V)$	$\gamma(V^{0.5})$	$V_{DSAT}(V)$	$k'(A/V^2)$	$\lambda(V^{-1})$
NMOS	0.43	0.4	0.63	115×10^{-6}	0.06
PMOS	-0.4	-0.4	-1	-30×10^{-6}	-0.1

$$\frac{(W/L)_p}{(W/L)_n} = \frac{115 \times 10^{-6}}{-30 \times 10^{-6}} \times \frac{0.63}{-1.0} \times \frac{(1.25 - 0.43 - 0.63/2)}{(1.25 - 0.4 - 1.0/2)} = 3.5$$
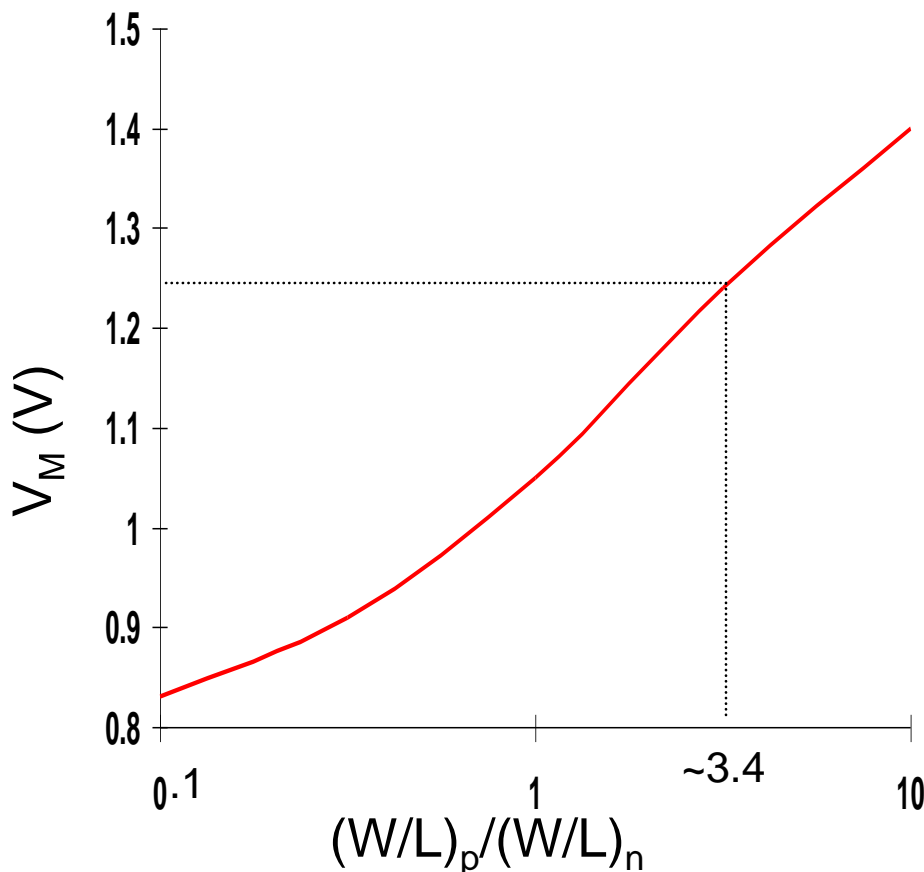
$$(W/L)_p = 3.5 \times 1.5 = 5.25 \text{ for a } V_M \text{ of } 1.25V$$



Note: x-axis is semilog


□ V_M is relatively insensitive to variations in device ratio

- setting the ratio to 3, 2.5 and 2 gives V_M 's of 1.22V, 1.18V, and 1.13V

□ Increasing the width of the PMOS moves V_M towards V_{DD}

□ Increasing the width of the NMOS moves V_M toward GND

۲- تحلیل حاشیه نویز

 

A piece-wise linear approximation of VTC

By definition, V_{IH} and V_{IL} are where $dV_{out}/dV_{in} = -1$ (= gain)

$$NM_H \equiv V_{DD} - V_{IH}$$
$$NM_L \equiv V_{IL} - GND$$

Approximating:

$$V_{IH} = V_M - V_M/g$$

$$V_{IL} = V_M + (V_{DD} - V_M)/g$$

So high gain in the transition region is very desirable

محاسبه گین در نقطه VM

$$k_n V_{DSATn} \left(V_{in} - V_{Tn} - \frac{V_{DSATn}}{2} \right) (1 + \lambda_n V_{out}) +$$
$$k_p V_{DSATp} \left(V_{in} - V_{DD} - V_{Tp} - \frac{V_{DSATp}}{2} \right) (1 + \lambda_p V_{out} - \lambda_p V_{DD}) = 0$$


با مشتق گرفتن از معادله فوق نسبت به V_{in}

$$\frac{dV_{out}}{dV_{in}} = - \frac{k_n V_{DSATn} (1 + \lambda_n V_{out}) + k_p V_{DSATp} (1 + \lambda_p V_{out} - \lambda_p V_{DD})}{\lambda_n k_n V_{DSATn} (V_{in} - V_{Tn} - V_{DSATn}/2) + \lambda_p k_p V_{DSATp} (V_{in} - V_{DD} - V_{Tp} - V_{DSATp}/2)}$$

تحلیل با تقریب


$$g = -\frac{1}{I_D(V_M)} \frac{k_n V_{DSATn} + k_p V_{DSATp}}{\lambda_n - \lambda_p}$$
$$\approx \frac{1+r}{(V_M - V_{Tn} - V_{DSATn}/2)(\lambda_n - \lambda_p)}$$

با جایگذاری $V_{in} = V_M$

 

بستگی شدید به پارامترهای تکنولوژی نظیر ضریب مدولاسیون طول کانال، ولتاژ آستانه و ولتاژ اشباع دارد.

 مقش طراح انتخاب V_M با سایز بندی مناسب ترانزیستورها است.




$0.25\mu\text{m}$, $(W/L)_p/(W/L)_n = 3.4$
 $(W/L)_n = 1.5$ (min size)
 $V_{DD} = 2.5\text{V}$

$V_M \approx 1.25\text{V}$, $g = -27.5$


$V_{IL} = 1.2\text{V}$, $V_{IH} = 1.3\text{V}$
 $NM_L = NM_H = 1.2$

 (actual values are
 $V_{IL} = 1.03\text{V}$, $V_{IH} = 1.45\text{V}$
 $NM_L = 1.03\text{V}$ & $NM_H = 1.05\text{V}$)




- Process variations (mostly) cause a shift in the switching threshold

Scaling the Supply Voltage


 


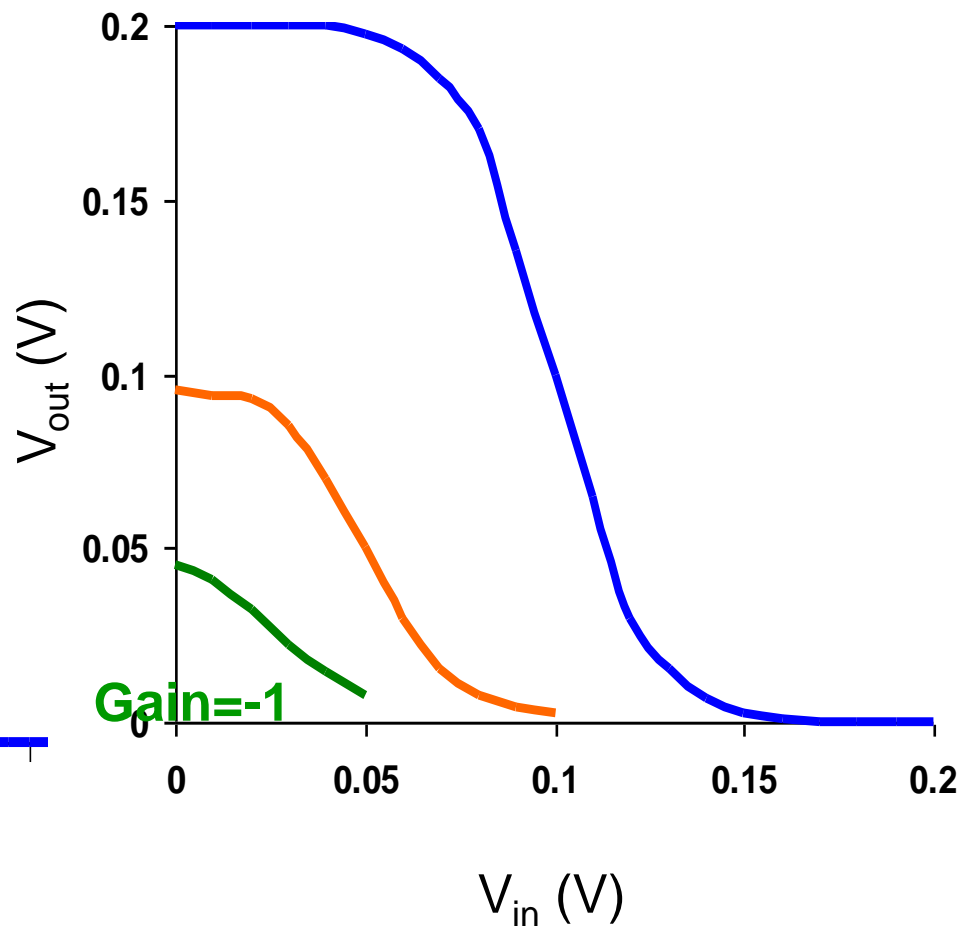Device threshold voltages are kept (virtually) constant




Device threshold voltages are kept (virtually) constant

  - مقدمه
- مشخصه انتقالی
- رفتار ایستا
- رفتار پویا
- تحلیل توان، انرژی و طراحی برای مصرف کم




- Gate response time is determined by the time to charge C_L through R_p (discharge C_L through R_n)

 - Propagation delay is proportional to the time-constant of the network formed by the pull-down resistor and the load capacitance



$$t_{pHL} = f(R_n, C_L)$$

 


$$t_{pHL} = \ln(2) R_{eqn} C_L = 0.69 R_{eqn} C_L$$

$$t_{pLH} = \ln(2) R_{eqp} C_L = 0.69 R_{eqp} C_L$$


$$V_{in} = V_{DD}$$

$$t_p = (t_{pHL} + t_{pLH})/2 = 0.69 C_L (R_{eqn} + R_{eqp})/2$$

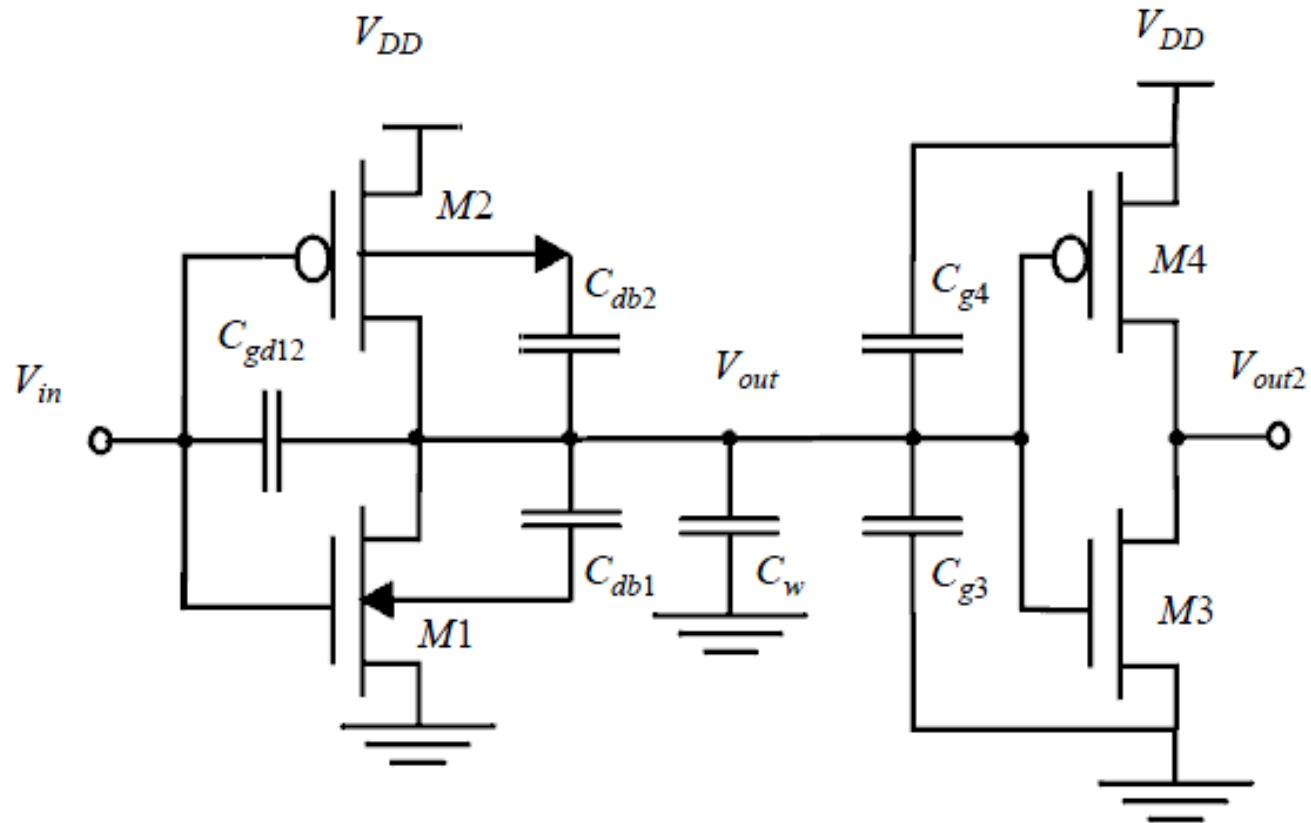- To equalize rise and fall times make the on-resistance of the NMOS and PMOS approximately equal.



 چون ترانزیستور M1 در ولتاژهای ورودی $0 > V_{DD}/2$ فقط در ناحیه قطع یا اشباع است فقط خازن Overlap داریم که آنهم با استفاده از اثر میلر می توان بین درین و زمین قرار داد.



$$C_{gd} = 2 C_{GD0} W$$

۲- برای دو ترانزیستور M1 و M2 خازن بین درین تا زمین وجود دارد که غیر خطی است و می توان یک خازم معادل با خطی سازی و تقریب در نظر گرفت. مقدار این خازن بستگی به سطح و محیط جانبی پیوند درین بدنه دارد.


$$C_{eq} = K_{eq} C_{j0}$$

۳- خازن ورودی طبقه بعد که بار Fanout این طبقه محسوب می شود.

$$\begin{aligned} C_{fanout} &= C_{gate}(\text{NMOS}) + C_{gate}(\text{PMOS}) \\ &= (C_{GSO_n} + C_{GDO_n} + W_n L_n C_{ox}) + (C_{GSO_p} + C_{GDO_p} + W_p L_p C_{ox}) \end{aligned}$$

۴- خازن اتصالات میانی CW

مثال محاسبه خازن های دو وارونگر cascade

 

تکنولوژی $0.25 \mu\text{m}$

$\lambda = 0.125 \mu\text{m}$

برای ترانزیستور NMOS

$$A_d = 4 \times 4 \lambda^2 + 3 \times 1 \lambda^2$$

$$P_d = (5 + 4 + 4 + 1 + 1) \lambda$$

برای ترانزیستور PMOS

$$A_d = 9 \times 4 \lambda^2 + 9 \times 1 \lambda^2$$


$$P_d = (5 + 9 + 5) \lambda$$

	W/L	AD (μm^2)	PD (μm)	AS (μm^2)	PS (μm)
NMOS	0.375/0.25	0.3 ($19 \lambda^2$)	1.875 (15λ)	0.3 ($19 \lambda^2$)	1.875 (15λ)
PMOS	1.125/0.25	0.7 ($45 \lambda^2$)	2.375 (19λ)	0.7 ($45 \lambda^2$)	2.375 (19λ)


Capacitor	Expression	Value (fF) (H→L)	Value (fF) (L→H)
C_{gd1}	$2 \text{CGD}0_n W_n$	0.23	0.23
C_{gd2}	$2 \text{CGD}0_p W_p$	0.61	0.61
C_{db1}	$K_{eqn} \text{AD}_n \text{CJ} + K_{eqsw_n} \text{PD}_n \text{CJSW}$	0.66	0.90
C_{db2}	$K_{eqp} \text{AD}_p \text{CJ} + K_{eqsw_p} \text{PD}_p \text{CJSW}$	1.5	1.15
C_{g3}	$(\text{CGD}0_n + \text{CGSO}_n) W_n + C_{ox} W_n L_n$	0.76	0.76
C_{g4}	$(\text{CGD}0_p + \text{CGSO}_p) W_p + C_{ox} W_p L_p$	2.28	2.28
C_w	From Extraction	0.12	0.12
C_L	Σ	6.1	6.0

مقدار مقاومت هنگام پر شدن (خالی شدن) خازن

 
با توجه به اینکه تاخیر انتشار با رسیدن به ۵۰٪ مقدار نهایی تعریف می شود.



(a) schematic

 

 (b) trajectory traversed on ID-VDS curve.



از مدل ترانزیستور به عنوان یک سویچ با تقریب معادله زیر استفاده می کنیم.

$$R_{eqn} = 3/4 V_{DD}/I_{DSATn}$$


با در نظر گرفتن مقاومت های on ترانزیستور های nMOS و pMOS با حداقل ابعاد معادل $13\text{ K}\Omega$ و $31\text{ K}\Omega$ (با توجه به اینکه عرض ترانزیستور های nMOS و pMOS فوق بترتیب ۱.۵ و ۴.۵ برابر حداقل ابعاد هستند. مقدار مقاومت های آنها با تقسیم مقاومت ترانزیستور مرجع به ضرایب فوق بدست می آید و لذا داریم .

$$t_{pHL} = 0.69 \times \left(\frac{13\text{k}\Omega}{1.5} \right) \times 6.1\text{fF} = 36\text{ psec}$$

$$t_{pLH} = 0.69 \times \left(\frac{31\text{k}\Omega}{4.5} \right) \times 6.0\text{fF} = 29\text{ psec}$$

$$t_p = \left(\frac{36 + 29}{2} \right) = 32.5\text{ psec}$$

Inverter Transient Response

 

$V_{DD} = 2.5V$
 $0.25\mu m$
 $W/L_n = 1.5$
 $W/L_p = 4.5$
 $R_{eqn} = 13\text{ k}\Omega (\div 1.5)$
 $R_{eqp} = 31\text{ k}\Omega (\div 4.5)$

$t_{pHL} = 36\text{ psec}$

$t_{pLH} = 29\text{ psec}$

so

$t_p = 32.5\text{ psec}$


From simulation: $t_{pHL} = 39.9\text{ psec}$ and $t_{pLH} = 31.7\text{ psec}$

□ با جایگزاری مقاومت معادل تقریبی

$$t_{pHL} = 0.69 R_{eqn} C_L$$

$$= 0.69 \left(\frac{3}{4} (C_L V_{DD}) / I_{DSATn} \right)$$

 
$$\approx 0.52 C_L / \left(\frac{W}{L}_n k'_n V_{DSATn} \right)$$



$$t_{pHL} = 0.69 \frac{3C_L V_{DD}}{4 I_{DSATn}} = 0.52 \frac{C_L V_{DD}}{\left(\frac{W}{L} \right)_n k'_n V_{DSATn} (V_{DD} - V_{Tn} - V_{DSATn} / 2)}$$

❑ Reduce C_L

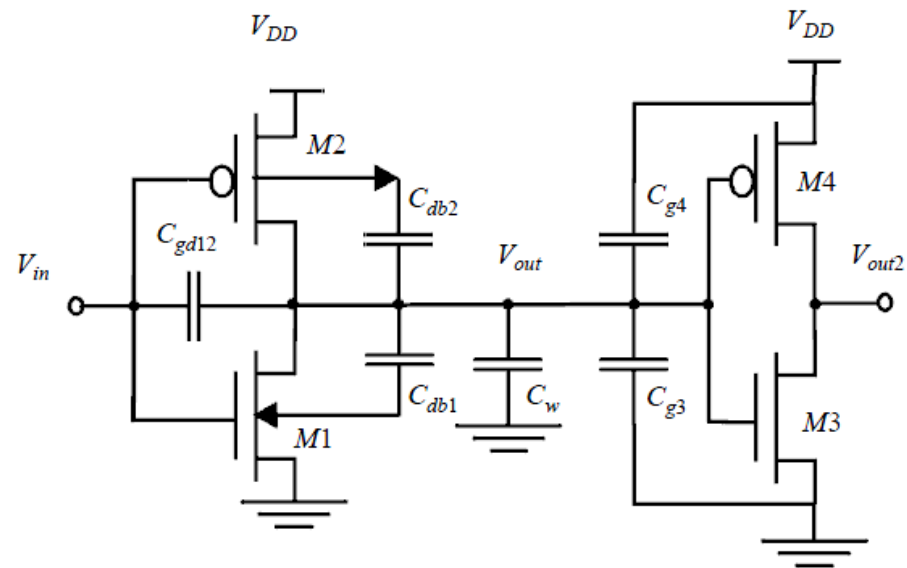- internal diffusion capacitance of the gate itself
 - keep the drain diffusion as small as possible
- interconnect capacitance
- Fanout (C_g Next Level)



- ❑ **Increase W/L ratio** of the transistor
 - the most powerful and effective performance optimization tool in the hands of the designer
 - watch out for **self-loading**! – when the intrinsic capacitance dominates the extrinsic load

- ❑ **Increase V_{DD}**
 - can trade-off energy for performance
 - increasing V_{DD} above a certain level yields only very minimal improvements
 - reliability concerns enforce a firm upper bound on V_{DD}


- ❑ So far have sized the PMOS and NMOS so that the R_{eq} 's match (ratio of 3 to 3.5)
 - symmetrical VTC
 - equal high-to-low and low-to-high propagation delays

- ❑ If speed is the only concern, **reduce** the width of the PMOS device!
 - widening the PMOS degrades the t_{pHL} due to larger parasitic capacitance

$$\beta = (W/L_p)/(W/L_n)$$

$r = R_{eqp}/R_{eqn}$ (resistance ratio of identically-sized PMOS and NMOS)
 
$$\beta_{opt} = \sqrt{r} \text{ when wiring capacitance is negligible}$$



β of 2.4 (= 31 k Ω /13 k Ω) gives symmetrical response

β of 1.6 to 1.9 gives optimal performance

□ Divide capacitive load, C_L , into

- C_{int} : intrinsic - diffusion and Miller effect
- C_{ext} : extrinsic - wiring and fanout


$$t_p = 0.69 R_{eq} C_{int} (1 + C_{ext}/C_{int}) = t_{p0} (1 + C_{ext}/C_{int})$$

- where $t_{p0} = 0.69 R_{eq} C_{int}$ is the intrinsic (**unloaded**) delay of the gate

□ Widening both PMOS and NMOS by a factor **S** reduces R_{eq} by an identical factor ($R_{eq} = R_{ref}/S$), but raises the **intrinsic** capacitance by the same factor ($C_{int} = SC_{iref}$)

$$t_p = 0.69 R_{ref} C_{iref} (1 + C_{ext}/(SC_{iref})) = t_{p0} (1 + C_{ext}/(SC_{iref}))$$

 - t_{p0} is independent of the sizing of the gate; *with no load the drive of the gate is totally offset by the increased capacitance*
- any S sufficiently larger than (C_{ext}/C_{int}) yields the best performance gains with least area impact



The majority of the improvement is already obtained for $S = 5$. Sizing factors larger than 10 barely yield any extra gain (and cost significantly more area).

self-loading effect
(intrinsic capacitance dominates)


- Extrinsic capacitance, C_{ext} , is a function of the fanout of the gate - the larger the fanout, the larger the external load.
- First determine the **input loading** effect of the inverter. Both C_g and C_{int} are proportional to the gate sizing, so $C_{int} = \gamma C_g$ is independent of gate sizing and

$$t_p = t_{p0} (1 + C_{ext} / \gamma C_g) = t_{p0} (1 + f / \gamma)$$

i.e., the delay of an inverter is a function of the ratio between its external load capacitance and its input gate capacitance: the **effective fan-out** f

$$f = C_{ext} / C_g$$

 □ حداقل کردن تاخیر با انتخاب مناسب تعداد بهینه و ابعاد بهینه وارونگر ها



the delay of the j-th inverter stage is

$$t_{p,j} = t_{p0} (1 + C_{g,j+1}/(\gamma C_{g,j})) = t_{p0}(1 + f_j/\gamma)$$

and
$$t_p = t_{p1} + t_{p2} + \dots + t_{pN}$$

$$t_p = \sum t_{p,j} = t_{p0} \sum (1 + C_{g,j+1}/(\gamma C_{g,j}))$$

□ می توان نشان داد حداقل میزان تاخیر وقتی اتفاق می افتد که $C_{g,j+1}/C_{g,j} = C_{g,j}/C_{g,j-1}$

□ به عبارت دیگر افزایش ابعاد طبقات نسبت به یکدیگر با نسبت ثابتی اتفاق بیافتد که در آن ضریب تناسب همان f است از رابطه زیر بدست می آید.

$$f = \sqrt[N]{C_L/C_{g,1}} = \sqrt[N]{F}$$


که در آن F نسبت خازن بار خروجی به خازن ورودی طبقه اول است.

$$(F = C_L/C_{g,1})$$

بنابراین حداقل تاخیر از رابطه زیر بدست می آید.

$$t_p = N t_{p0} (1 + \sqrt[N]{F})$$

 N تعداد طبقات است بنابراین می توان N مناسب را انتخاب نمود تا تاخیر بهینه شود.



$C_L/C_{g,1}$ has to be evenly distributed over $N = 3$ inverters \square

$$C_L/C_{g,1} = 8/1$$

$$f = \sqrt[3]{8} = 2$$

□ اگر تعداد طبقات را زیاد کنیم بدلیل تاخیر ذاتی که در N ضرب می شود تاخیر زیاد می شود



□ اگر تعداد طبقات را کم بگیریم تاخیر ناشی از Fanout غالب می شود.

□ مقدار بهینه از حل معادله زیر بدست می آید.

$$\gamma + \sqrt{F} - (\sqrt{F} \ln F)/N = 0$$





□ For $\gamma = 0$ $N = \ln(F)$ and the *effective-fan out becomes* $f = e = 2.71828$

  □ For $\gamma = 1$ (the typical case) the optimum effective fan-out (tapering factor) turns out to be close to 3.6



- ❑ Choosing f larger than optimum has little effect on delay and reduces the number of stages (and area).
 - Common practice to use $f = 4$ (for $\gamma = 1$)
 - But **too many** stages has a substantial negative impact on delay

Example of Inverter (Buffer) Staging

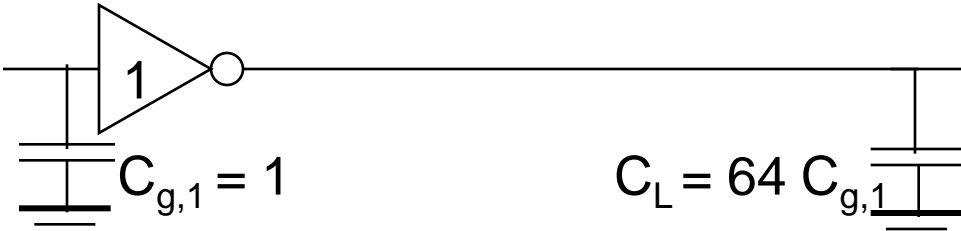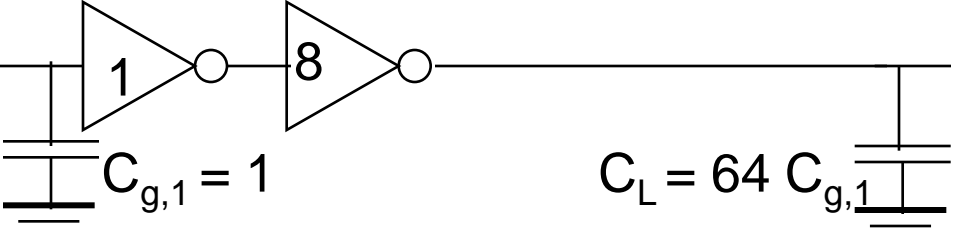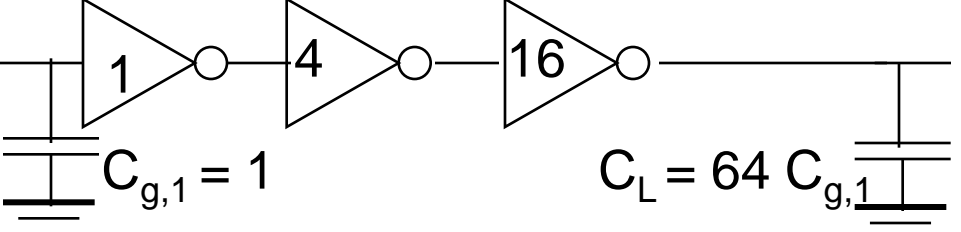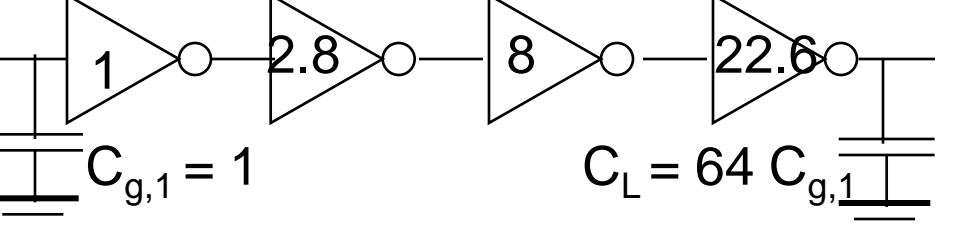
	N	f	t_p
	1	64	65
	2	8	18
	3	4	15
	4	2.8	15.3

Impact of Buffer Staging for Large C_L

F ($\gamma = 1$)	Unbuffered	Two Stage Chain	Opt. Inverter Chain
10	11	8.3	8.3
100	101	22	16.5
1,000	1001	65	24.8
10,000	10,001	202	33.1

- ❑ Impressive speed-ups with optimized cascaded inverter chain for very large capacitive loads.

$$C_L = 64 C_{g,1}$$

 


Hints: Determine first the ratio's between the devices that minimize the delay. You should find that the following must hold,

$$\frac{4C_{g,2}}{C_{g,1}} = \frac{4C_{g,3}}{C_{g,2}} = \frac{C_L}{C_{g,3}}$$

Finding the actual gate sizes ($C_{g,3} = 2.52C_{g,2} = 6.35C_{g,1}$) is a relatively straightforward task. Straightforward sizing of the inverter chain, without taking the fanout into account, would have led to a sizing factor of 4 instead of 2.52.

 
- ❑ In reality, the **input** signal changes gradually (and both PMOS and NMOS conduct for a brief time). This affects the current available for charging/discharging C_L and impacts propagation delay.
- ❑ t_p increases **linearly** with increasing input slope, t_s , once $t_s > t_p$
- ❑ t_s is due to the limited driving capability of the preceding gate



for a minimum-size inverter
with a fan-out of a single gate


- مقدمه
- مشخصه انتقالی
- رفتار ایستا
- رفتار پویا
- تحلیل توان، انرژی و طراحی برای مصرف کم

 • تلفات دینامیکی : در اثر سویچینگ و مصرف انرژی برای شارژ و دشارژ خازن بار



• تلفات ناشی از مسیر جریان مستقیم

 • تلفات استاتیک (جریان نشتی و زیر آستانه)




ساختار وارونگر CMOS استاتیک بگونه ای است که تلفات توان استاتیک در آن ناچیز است و عمده تلفات در حالت تغییر وضعیت از 0 به 1 یا بر عکس اتفاق می افتد. هر بار که خازن بار از مسیر pMOS شارژ می شود ولتاژ آن از 0 به VDD می رسد.

انرژی صرف شده توسط منبع VDD و انرژی ذخیره شده در خازن را می توان با روابط زیر بترتیب نشان داد.

$$E_{VDD} = \int_0^{\infty} i_{VDD}(t) V_{DD} dt = V_{DD} \int_0^{\infty} C_L \frac{dv_{out}}{dt} dt = C_L V_{DD} \int_0^{V_{DD}} dv_{out} = C_L V_{DD}^2$$

$$E_C = \int_0^{\infty} i_{VDD}(t) v_{out} dt = \int_0^{\infty} C_L \frac{dv_{out}}{dt} v_{out} dt = C_L \int_0^{V_{DD}} v_{out} dv_{out} = \frac{C_L V_{DD}^2}{2}$$

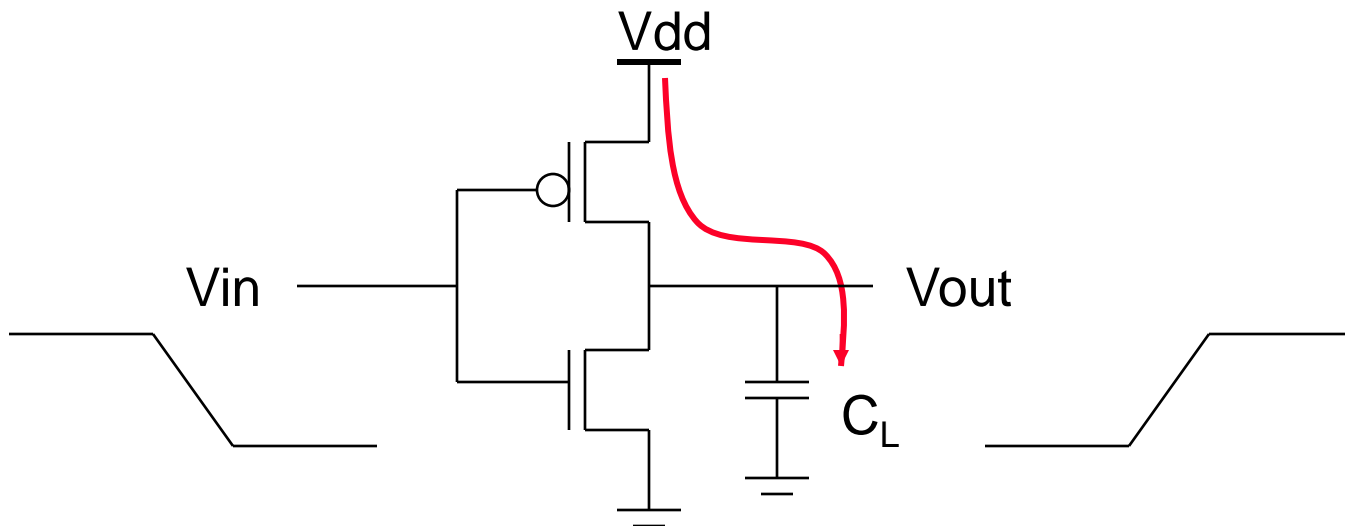فقط نیمی از انرژی گرفته شده از منبع در خازن بار ذخیره می شود و نیم دیگر آن در ترانزیستور pMOS تلف می شود. میزان تلفات بستگی به ابعاد (مقاومت) ترانزیستور pMOS ندارد. در سیکل دشارژ انرژی ذخیره شده در خازن در ترانزیستور nMOS تلف می شود. بنابر این انرژی تلف شده در هر سیکل برابر $C_L V_{DD}^2$ می شود.



$$\text{Energy/transition} = C_L * V_{DD}^2 * P_{0 \rightarrow 1} \quad f_{0 \rightarrow 1}$$

$$P_{\text{dyn}} = \text{Energy/transition} * f = C_L * V_{DD}^2 * P_{0 \rightarrow 1} * f$$

$$P_{\text{dyn}} = C_{\text{EFF}} * V_{DD}^2 * f \quad \text{where } C_{\text{EFF}} = P_{0 \rightarrow 1} C_L$$

Not a function of transistor sizes!

Data dependent - a function of **switching activity!**

طراحی برای مصرف کم

با توجه به معادله توان دینامیکی ۳ عامل در کاهش توان موثر هستند

کاهش ولتاژ تغذیه: چون توان مصرفی با توان دوم ولتاژ متناسب است این عامل مهمی است با کاهش ولتاژ تاخیر گیت زیاد می شود. بنابراین یک trade off بین توان و تاخیر وجود دارد

کاهش خازن بار: چون کاهش خازن موثر هم تلفات و هم تاخیر را کاهش می دهد کاهش آن مطلوب است. اما در عمل چون بخش عمده ای از خازن بار خازنهای داخلی ترانزیستور مثل خازن گیت و نفوذ هستند کاهش خازن ها به معنی کوچک سازی ترانزیستور است که به نوبه خود چون مقاومت معادل آنها را افزایش می دهد منجر به افزایش تاخیر می شود.

کاهش احتمال سویچینگ این موضوع را با معماری مناسب مدار تا حدی می توان انجام داد و در فصل های آتی به آن اشاره می شود

کاهش فرکانس: معمولا بر خلاف میل طراح است. (گیت کردن کلاک سیگنال های غیر فعال) در عمل ترکیبی از کاهش ولتاژ تغذیه و انتخاب مناسب ابعاد گیت جهت بهینه سازی توان و همزمان جلوگیری از افزایش تاخیر بیش از حد مطلوب مورد استفاده قرار می گیرد. در شبکه های بزرگ توجه به ابعاد موثر و کاهش ولتاژ تغذیه می تواند مصرف توان را تا ۱۰ برابر کاهش دهد.

Capacitance:
Function of fan-out,
wire length, transistor
sizes

Supply Voltage:
Has been dropping
with successive
generations



$$P_{\text{dyn}} = C_L V_{\text{DD}}^2 P_{0 \rightarrow 1} f$$

Activity factor:
How often, on average,
do wires switch?

Clock frequency:
Increasing...

تلفات ناشی از مسیر جریان مستقیم

  در حالت گذرا چون شیب سیگنال ورودی محدود است برای مدت کمی یک مسیر جریان مستقیم بین V_{DD} و زمین ایجاد می شود.



$$E_{dp} = V_{DD} \frac{I_{peak} t_{sc}}{2} + V_{DD} \frac{I_{peak} t_{sc}}{2} = t_{sc} V_{DD} I_{peak} \quad t_{sc} = \frac{V_{DD} - 2V_T}{V_{DD}} t_s \approx \frac{V_{DD} - 2V_T}{V_{DD}} \times \frac{t_{r(f)}}{0.8}$$

$$E_{sc} = t_{sc} V_{DD} I_{peak} P_{0 \rightarrow 1}$$

$$P_{sc} = t_{sc} V_{DD} I_{peak} f_{0 \rightarrow 1}$$

I_{peak} determined by


the saturation current of the P and N transistors
which depend on their sizes, process technology,
temperature, etc.

strong function of the ratio between input and output
slopes

a function of C_L

اثر خازن بار روی تلفات مسیر جریان مستقیم

 
در حالتیکه تاخیر گیت زیاد باشد، وقتی سیگنال ورودی تغییر می کند ولتاژ خروجی هنوز بالاست، لذا اختلاف پتانسیل سورس و درین pMOS ناچیز است و جریان اتصال کوتاه ناچیز خواهد بود. در عوض اگر خازن بار کوچک باشد و تاخیر گیت کم باشد. ولتاژ درین سورس سریع تغییر می کند و لذا جریان اتصال کوتاه زیاد خواهد بود



 (a) Large capacitive load

Large capacitive load

Output fall time significantly larger than input rise time.




(b) Small capacitive load

Small capacitive load

Output fall time substantially smaller than the input rise time.


جریان اتصال کوتاه بر حسب خازن بار

 

When load capacitance is small, I_{peak} is large.

Short circuit dissipation is minimized by matching the rise/fall times of the input and output signals - **slope engineering**.

P_{sc} as a Function of Rise/Fall Times

 

When load capacitance is small ($t_{sin}/t_{sout} > 2$ for $V_{DD} > 2V$) the power is dominated by P_{sc}

If $V_{DD} < V_{Tn} + |V_{Tp}|$ then P_{sc} is eliminated since both devices are never on at the same time.


$$W/L_p = 1.125 \mu\text{m}/0.25 \mu\text{m}$$

$$W/L_n = 0.375 \mu\text{m}/0.25 \mu\text{m}$$

$$C_L = 30 \text{ fF}$$

در حالت استاتیک به دلیل وجود جریان نشتی پیوند های بایاس معکوس درین و سورس با بدنه تلفات ایستایی داریم. در عمل این تلفات ناچیز است و در حد $10-100 \text{ pA}/\mu\text{m}^2$ است. اما این جریان نشتی با افزایش دما بصورت نمایی زیاد می شود و به عنوان نمونه در دمای 85°C حدود ۶۰ برابر دمای اطاق می شود.

 همینطور تلفات ناشی از جریان زیر آستانه برای ترانزیستور ها در حالت خاموش وجود دارد.




$$P_{stat} = I_{stat}V_{DD}$$

Why worry about power? -- Standby Power

Year	2002	2005	2008	2011	2014
Power supply V_{dd} (V)	1.5	1.2	0.9	0.7	0.6
Threshold V_T (V)	0.4	0.4	0.35	0.3	0.25

 - Drain leakage will increase as V_T decreases to maintain noise margins and meet frequency demands, leading to excessive **battery draining standby** power consumption.




...and phones leaky!



Source: Borkar, De Intel®

 - Continued scaling of supply voltage and the subsequent scaling of threshold voltage will make subthreshold conduction a dominant component of power dissipation.




- An 90mV/decade V_T roll-off - so each 255mV increase in V_T gives 3 orders of magnitude reduction in leakage (but adversely affects performance)

TSMC Processes Leakage and V_T

	CL018 G	CL018 LP	CL018 ULP	CL018 HS	CL015 HS	CL013 HS
V_{dd}	1.8 V	1.8 V	1.8 V	2 V	1.5 V	1.2 V
T_{ox} (effective)	42 Å	42 Å	42 Å	42 Å	29 Å	24 Å
L_{gate}	0.16 μm	0.16 μm	0.18 μm	0.13 μm	0.11 μm	0.08 μm
I_{DSat} (n/p) ($\mu\text{A}/\mu\text{m}$)	600/260	500/180	320/130	780/360	860/370	920/400
I_{off} (leakage) ($\rho\text{A}/\mu\text{m}$)	20	1.60	0.15	300	1,800	13,000
V_{Tn}	0.42 V	0.63 V	0.73 V	0.40 V	0.29 V	0.25 V
FET Perf. (GHz)	30	22	14	43	52	80

Exponential Increase in Leakage Currents

 

From De, 1999

$$E = C_L V_{DD}^2 P_{0 \rightarrow 1} + t_{sc} V_{DD} I_{peak} P_{0 \rightarrow 1} + V_{DD} I_{leakage}$$

$$f_{0 \rightarrow 1} = P_{0 \rightarrow 1} * f_{clock}$$

$$P = C_L V_{DD}^2 f_{0 \rightarrow 1} + t_{sc} V_{DD} I_{peak} f_{0 \rightarrow 1} + V_{DD} I_{leakage}$$

Dynamic power
(~90% today and
decreasing
relatively)

Short-circuit
power
(~8% today and
decreasing
absolutely)

Leakage power
(~2% today and
increasing)

$$P_{tot} = P_{dyn} + P_{dp} + P_{stat} = (C_L V_{DD}^2 + V_{DD} I_{peak} t_s) f_{0 \rightarrow 1} + V_{DD} I_{leak}$$

حاصلضرب توان در تاخیر و انرژی در تاخیر

پارامتر PDP که حاصلضرب توان در تاخیر است. این پارامتر معیاری از میزان انرژی مصرفی می باشد. اگر از تلفات استاتیک و تلفات مسیر جریان مستقیم صرفنظر کنیم می توان دید PDP معادل انرژی مصرفی گیت بازای یک سویچینگ می باشد.

$$PDP = C_L V_{DD}^2 f_{max} t_p = \frac{C_L V_{DD}^2}{2}$$

پارامتر قابل توجه دیگر حاصلضرب انرژی در تاخیر می باشد که معیاری از سرعت و انرژی گیت است.

$$EDP = PDP \times t_p = P_{av} t_p^2 = \frac{C_L V_{DD}^2}{2} t_p \quad t_p \approx \frac{\alpha C_L V_{DD}}{V_{DD} - V_{Te}} \quad V_{Te} = V_T + V_{DSAT}/2$$

$$EDP = \frac{\alpha C_L^2 V_{DD}^3}{2(V_{DD} - V_{TE})}$$

مثال: ولتاژ تغذیه بهینه

$$V_{DDopt} = \frac{3}{2}V_{TE}$$

$$V_{In} = 0.43 \text{ V}, V_{Dsatn} = 0.63 \text{ V}, V_{TEn} = 0.74 \text{ V}.$$


$$V_{Itp} = -0.4 \text{ V}, V_{Dsatp} = -1 \text{ V}, V_{TEp} = -0.9 \text{ V}.$$

$$V_{TE} \approx (V_{TEn} + |V_{TEp}|) / 2 = 0.8 \text{ V}$$


$$V_{DDopt} = (3/2) \times 0.8 \text{ V} = 1.2 \text{ V}.$$

- EDP is the average **energy** consumed multiplied by the computation time required
- takes into account that one can **trade** increased delay for lower energy/operation (e.g., via supply voltage scaling that increases delay, but decreases energy consumption)


محاسبه ولتاژ بهینه برای حداقل کردن EDP

 

 ❑ Which design is the “best” (fastest, coolest, both) ?



	Constant Throughput/Latency		Variable Throughput/Latency	
Energy	Design Time	Non-active Modules	Run Time	
Active	Logic Design Reduced V_{dd} Sizing Multi- V_{dd}	Clock Gating	DFS, DVS (Dynamic Freq, Voltage Scaling)	
Leakage	+ Multi- V_T	Sleep Transistors Multi- V_{dd} Variable V_T	+ Variable V_T	

 

□ Goal: Minimize Energy of whole circuit

- Design parameters: f and V_{DD}
- $t_p \leq t_{pref}$ of circuit with $f=1$ and $V_{DD}=V_{ref}$

$$t_p = t_{p0} \left(\left(1 + \frac{f}{\gamma} \right) + \left(1 + \frac{F}{f\gamma} \right) \right)$$

$$t_{p0} \propto \frac{V_{DD}}{V_{DD} - V_{TE}}$$

□ Performance Constraint ($\gamma=1$)


$$\frac{t_p}{t_{pref}} = \frac{t_{p0}}{t_{p0ref}} \frac{\left(2 + f + \frac{F}{f}\right)}{(3 + F)} = \frac{V_{DD}}{V_{ref}} \frac{V_{ref} - V_{TE}}{V_{DD} - V_{TE}} \frac{\left(2 + f + \frac{F}{f}\right)}{(3 + F)} = 1$$

□ Energy for single Transition


$$E = V_{DD}^2 C_{g1} [(1 + \gamma)(1 + f) + F]$$

$$\frac{E}{E_{ref}} = \left(\frac{V_{DD}}{V_{ref}}\right)^2 \left(\frac{2 + 2f + F}{4 + F}\right)$$


$$V_{DD} = f(f)$$

 

$$E/E_{ref} = f(f)$$

 

- Device sizing affects dynamic energy consumption
 - gain is largest for networks with large overall effective fan-outs ($F = C_L/C_{g,1}$)
- The optimal gate sizing factor (f) for dynamic energy is smaller than the one for performance, especially for large F 's
 - e.g., for $F=20$,
 $f_{\text{opt}}(\text{energy}) = 3.53$ while
 $f_{\text{opt}}(\text{performance}) = 4.47$
- If energy is a concern avoid oversizing beyond the optimal

 

□ Prime choice: Reduce voltage!

- Recent years have seen an acceleration in supply voltage reduction (USE Multi VDD)


□ Reduce switching activity (How?)

□ Reduce physical capacitance

- Device Sizing: for $F=20$

- $f_{opt}(\text{energy})=3.53$, $f_{opt}(\text{performance})=4.47$

 
- ❑ Decreasing the V_{DD} **decreases** dynamic energy consumption (quadratically)
- ❑ But, **increases** gate delay (decreases performance)



- ❑ Determine the critical path(s) at **design time** and use high V_{DD} for the transistors on those paths for speed. Use a lower V_{DD} on the other gates, especially those that drive large capacitances (as this yields the largest energy benefits).


Multi V_T

 - ❑ Reducing the V_T **increases** the sub-threshold leakage current (exponentially)
 - 90mV reduction in V_T increases leakage by an order of magnitude
- ❑ But, reducing V_T **decreases** gate delay (increases performance)



- ❑ Determine the critical path(s) at **design time** and use low V_T devices on the transistors on those paths for speed. Use a high V_T on the other logic for leakage control.
 - A careful assignment of V_T 's can reduce the leakage by as much as 80%

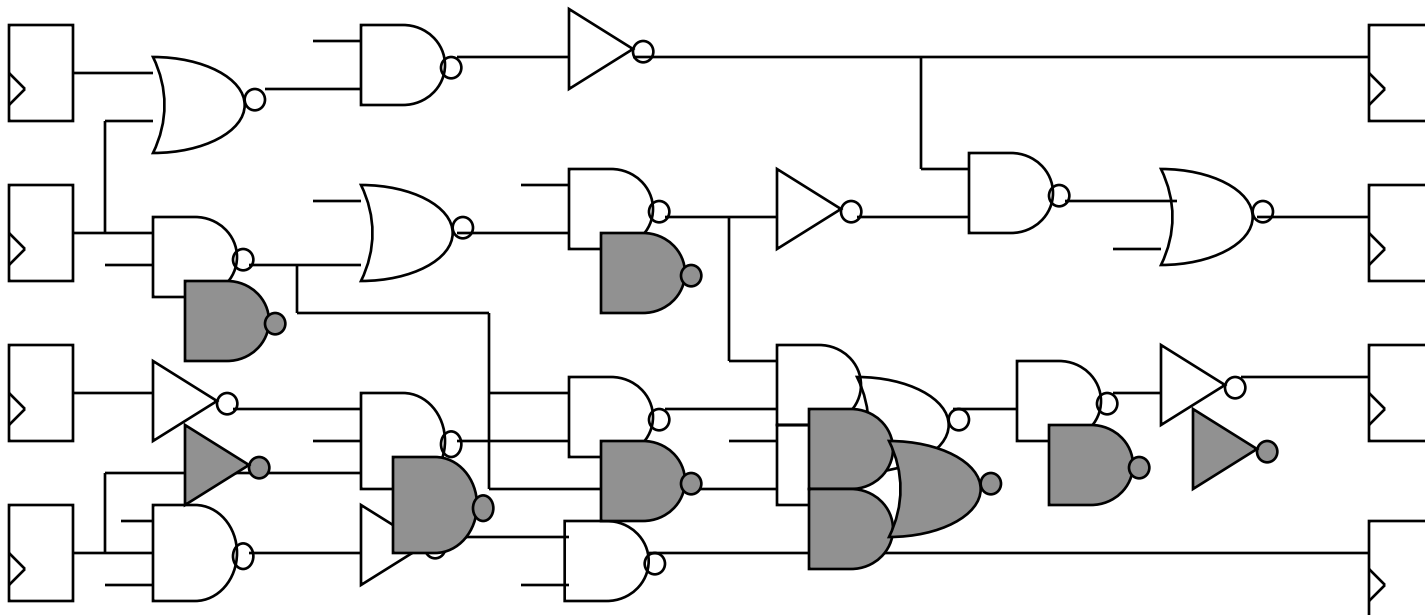- ❑ Minimum energy consumption is achieved if **all** logic paths are critical (have the same delay)
- ❑ Use lower threshold on timing-critical paths
 - Assignment can be done on a per gate or transistor basis;



Variable V_T (ABB)


□ $V_T = V_{T0} + \gamma(\sqrt{|-2\phi_F + V_{SB}|} - \sqrt{|-2\phi_F|})$

□ For an n-channel device, the substrate is normally tied to ground ($V_{SB} = 0$)

□ A negative bias on V_{SB} causes V_T to increase

□ Adjusting the substrate bias at **run time** is called **adaptive body-biasing (ABB)**

- Requires a dual well fab process

 

V_{SB} (V)

- ❑ Switching activity, $P_{0 \rightarrow 1}$, has two components
 - A static component – function of the logic topology
 - A dynamic component – function of the timing behavior (glitching)

2-input NOR Gate

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

Static transition probability

$$P_{0 \rightarrow 1} = P_{\text{out}=0} \times P_{\text{out}=1}$$

$$= P_0 \times (1 - P_0)$$

With input **signal probabilities**

$$P_{A=1} = 1/2$$

$$P_{B=1} = 1/2$$

NOR static transition probability

$$= 3/4 \times 1/4 = 3/16$$


❑ Switching activity is a strong function of the input signal statistics

- P_A and P_B are the probabilities that inputs A and B are one

With input **signal probabilities**

$$P_{A=1} = 1/2$$

$$P_{B=1} = 1/2$$

 


A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

$$P_{0 \rightarrow 1} = P_0 \times P_1 = (1 - (1 - P_A)(1 - P_B)) (1 - P_A)(1 - P_B)$$

Transition Probabilities for Some Basic Gates

	$P_{0 \rightarrow 1} = P_{\text{out}=0} \times P_{\text{out}=1}$
NOR	$(1 - (1 - P_A)(1 - P_B)) \times (1 - P_A)(1 - P_B)$
OR	$(1 - P_A)(1 - P_B) \times (1 - (1 - P_A)(1 - P_B))$
NAND	$P_A P_B \times (1 - P_A P_B)$
AND	$(1 - P_A P_B) \times P_A P_B$
XOR	$(1 - (P_A + P_B - 2P_A P_B)) \times (P_A + P_B - 2P_A P_B)$

 


For X: $P_{0 \rightarrow 1} = P_0 \times P_1 = (1 - P_A) P_A$

$= 0.5 \times 0.5 = 0.25$

For Z: $P_{0 \rightarrow 1} = P_0 \times P_1 = (1 - P_X P_B) P_X P_B$

$= (1 - (0.5 \times 0.5)) \times (0.5 \times 0.5) = 3/16$

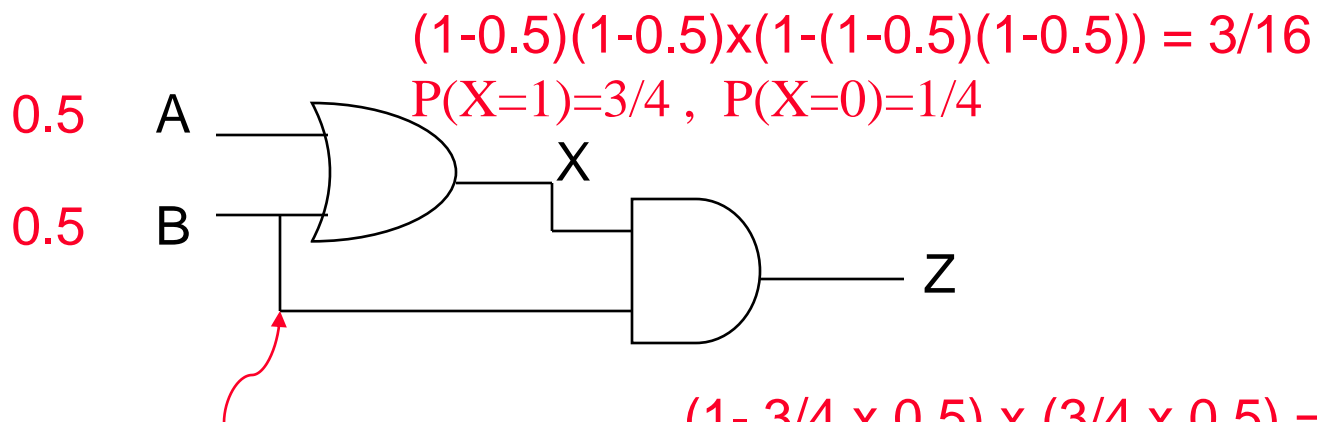- Determining switching activity is complicated by the fact that signals exhibit correlation in space and time
 - reconvergent fan-out



Reconvergent

$$P(Z=1) = P(B=1) \& P(A=1 \text{ OR } B=1)$$

$$Z=(A+B)B=AB+B=B(1+A)=B \quad P(Z=1)=1/2 \quad P(0>1)=1/4$$

- Have to use **conditional probabilities**


- Logic restructuring: changing the topology of a logic network to reduce transitions

AND: $P_{0 \rightarrow 1} = P_0 \times P_1 = (1 - P_A P_B) \times P_A P_B$


$(1 - 0.25) \times 0.25 = 3/16,$

$P(W=1) = 1/4$

$7/64, P(X=1) = 1/8$

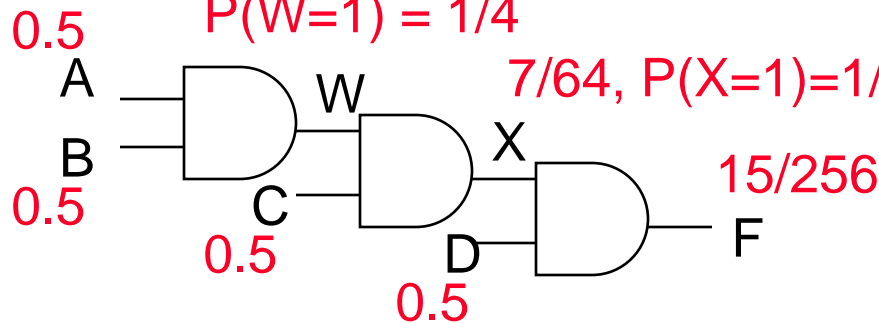


$\Sigma = 0.355$

 


$\Sigma = 0.433$

 Chain implementation has a lower overall switching activity than the tree implementation for random inputs



$\Sigma = 0.1$

 

$\Sigma = 0.0296$

Beneficial to postpone the introduction of signals with a **high** transition rate (signals with signal probability close to 0.5)

□ درس بعدی

● گیت های ترکیبی